

ECE 551


HW3 Solution



HW3 Problem 1 (20pts) SM Design


A Single Slope A2D converter (capable of averaging 8 samples) was discussed in Lecture1. The block diagram is shown below. On the course webpage under HW3 you will find files:

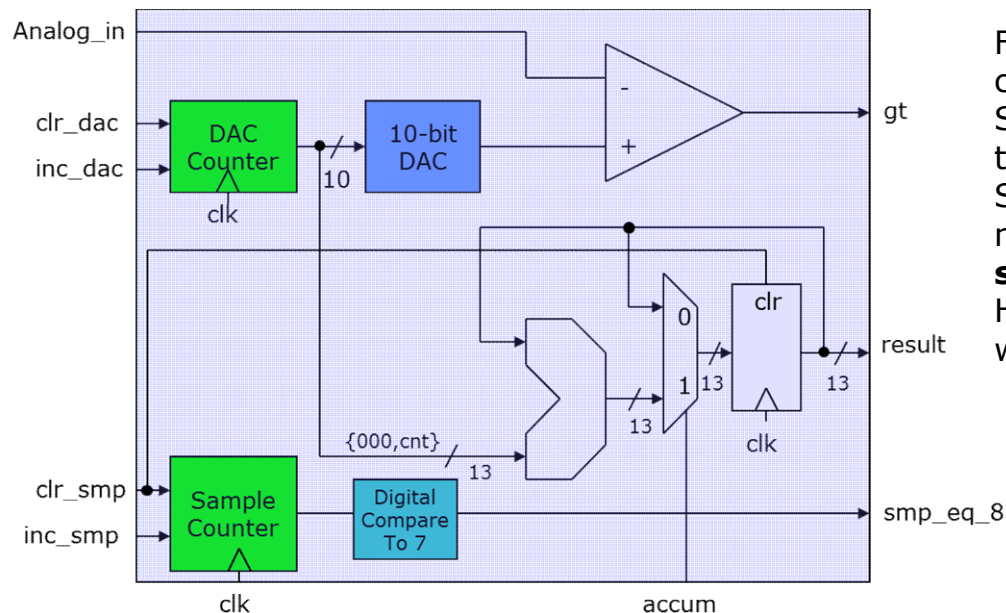ss_A2D_tb.v, ss_A2D.v, ss_A2D_datapath.v, ss_A2D_SM_shell.sv.



Flush out **ss_A2D_SM_shell.sv** to complete the control (state machine). Simulate your resulting design using the provided self checking test bench. Submit your verilog for the state machine (file should be called **ss_A2D_SM.sv** to the dropbox for HW3). Also submit proof that it worked.

 Hierarchy of design is as shown. Testbench instantiates DUT (ss_A2D). Which in turn instantiates datapath and statemachine. You are simply flushing out the SM code and renaming the file from ss_A2D_SM_shell.sv to ss_A2D_SM.sv. You are also simulating to prove it works.



```

module ss_A2D_SM(clk,rst_n,strt_cnv,smp_eq_8,gt,clr_dac,inc_dac,
                 clr_smp,inc_smp,accum,cnv_cmplt);

    input clk,rst_n;           // clock and asynch reset
    input strt_cnv;           // asserted to kick off a conversion
    input smp_eq_8;           // from datapath, tells when we have 8 samples
    input gt;                 // gt signal, has to be double flopped

    output clr_dac;           // clear the input counter to the DAC
    output inc_dac;           // increment the counter to the DAC
    output clr_smp;           // clear the sample counter
    output inc_smp;           // increment the sample counter
    output accum;             // asserted to make accumulator accumulate sample
    output cnv_cmplt;         // indicates when the conversion is complete

    typedef enum reg [1:0] {IDLE,CONV,ACCUM} state_t;

    state_t state,nstate;     // both state and nstate of the enum state type
    reg gt_ff1, gt_ff2;       // flops for gt metastability purposes

    //// All signals that are outputs of SM are of type logic ////
    logic clr_dac,inc_dac,clr_smp,inc_smp,accum,cnv_cmplt;

    //// Infer state flops next ////
    always_ff @(posedge clk, negedge rst_n)
        if (!rst_n)
            state <= IDLE;
        else
            state <= nstate;

```

See next Slide for rest

```

//// flop gt twice for meta-stability purposes ////
always @(posedge clk)
    if (clr_dac) begin
        gt_ff1 <= 1'b0;
        gt_ff2 <= 1'b0;
    end else begin
        gt_ff1 <= gt;
        gt_ff2 <= gt_ff1;
    end
end

always_comb begin
    //// default all outputs ////
    clr_dac = 0;
    inc_dac = 0;
    clr_smp = 0;
    inc_smp = 0;
    accum = 0;
    cnv_cmplt = 0;
    nstate = IDLE;

    case (state)
        IDLE : if (strt_cnv) begin
            clr_dac = 1;
            clr_smp = 1;
            nstate = CONV;
        end
        CONV : if (!gt_ff2) begin
            inc_dac = 1;
            nstate = CONV;
        end else begin
            accum = 1;
            nstate = ACCUM;
        end
        default : if (smp_eq_8) begin // this is the accum state
            cnv_cmplt = 1;
            nstate = IDLE;
        end else begin
            clr_dac = 1;
            inc_smp = 1;
            nstate = CONV;
        end
    end
endcase
end

```

HW3 Problem 2 (25pts) ESC Interface

In the vicinity of slide 38 of the Project Spec you will find a section on ESC (Electronic Speed Control). Read these slides carefully.

You will be implementing the ESC controller, with the following interface:


Signal:	Dir:	Description:
clk	in	50MHz clock
rst_n	in	Active low asynch reset
SPEED[10:0]	in	Result from speed sensor
OFF[9:0]	in	Offset in ESC/motor pairs. Give all pairs a close to the same speed. This offset is
PWM		motor speed. It is effectively a PWM signal.

- If both SPEED and OFF are 0, the PWM width is 1ms.
- For every count in SPEED or OFF the speed would increase by 0.32usec

This problem will have been completed as part of in class exercises. Just submit your ESC_interface.sv that was checked off in class.

Every one demoed a working version of this on their DE0-Nano boards, so perhaps your code is not pretty, but it works and synthesizes....no solution provided

 Pulse width determines motor speed, 1ms = slowest/stopped
2ms = fastest




Pulses come at $\approx 20\text{ms}$ rate (50Hz)

What is UART (RS-232)


- RS-232 signal phases

 - Idle
- Start bit
- Data (8-data for our project)
- Parity (no parity for our project)
- Stop bit – channel returns to Idle
- Idle or Start next




- Receiver monitors for falling edge of Start bit. Counts off 1.5 bit times and starts shifting (right shifting since LSB is first) data into a register.
- Transmitter sits idle till told to transmit. Then will shift out a 9-bit (start bit appended) register at the baud rate interval.

UART Receiver/Transmitter

 

A host computer will send commands to the Logic Analyzer via a UART serial peripheral


Signal:	Dir:	Description
clk,rst_n	in	100MHz system clock & active low reset
RX	in	Serial data carrying command from host computer
rdy	out	Asserted when a byte has been received. Falls when new start bit comes, or when <i>clr_rdy</i> knocks it down.
cmd[7:0]	out	Byte received (serves as command to LA)
clr_rdy	in	Asserted to knock down the rdy signal.

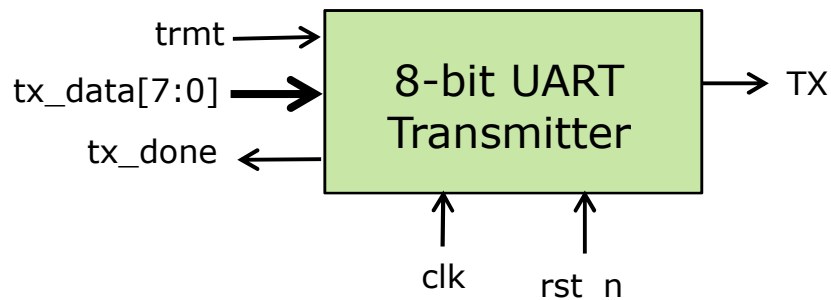

The follower sends responses back to the host computer. These responses are sent via a UART serial peripheral.

Signal:	Dir:	Description
clk,rst_n	in	100MHz system clock & active low reset
TX	out	Serial data output back to host
trmt	in	Asserted for 1 clock to initiate transmission
tx_data[7:0]	in	Byte to transmit (response from LA)
tx_done	out	Asserted when byte is done transmitting. Stays high till next byte transmitted.

Possible Topology of UART_tx

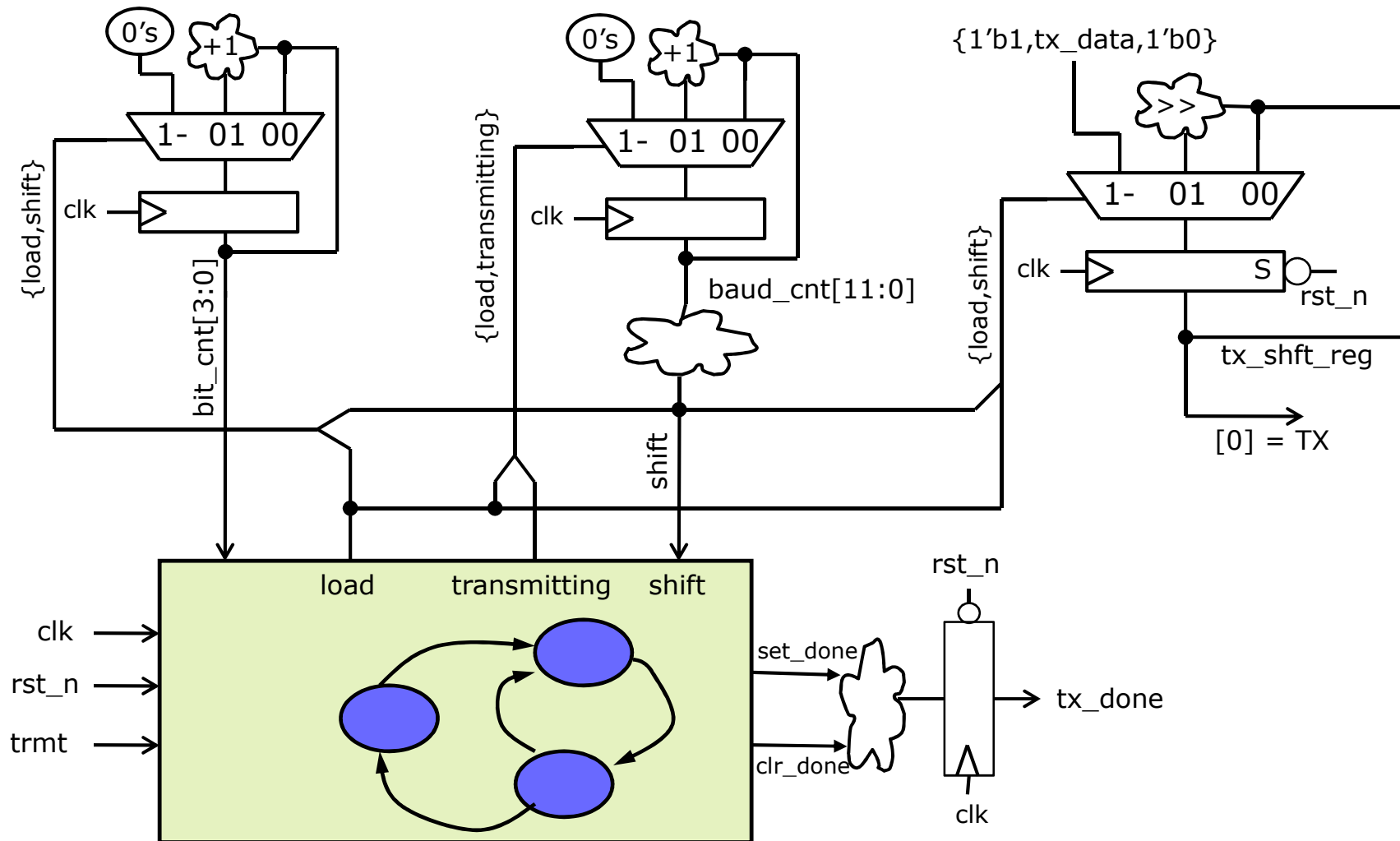

HW3 Problem 3 (20pts) UART Transmitter

Implement a the UART Transmitter (**UART_tx.sv**).

Make a simple test bench for it. This is one instance in which I would not spend too much time on the test bench. You can just instantiate your transmitter and send a few bytes. Verify the correct functionality (including baud rate) by staring at the green waveforms. You will make a more comprehensive test bench in the next problem.

Submit **UART_tx.sv** to the dropbox for HW3.

HW3 Problem 4 (25pts + 10pts) UART Receiver

Implement a the UART Receiver (**UART_rcv.sv**).

Since you have a transmitter too, it is now easy to make a self checking test bench. Architect the test bench as shown. Does the 8-bit value you transmit match the value you receive when the transmission completes?

Submit **UART_rcv.sv** and your test bench to the dropbox for HW3.

