

ECE 551

Digital Design And Synthesis

Fall '17

Behavioral Verilog

 always & initial blocks
 Coding flops

 if else & case statements

Blocking vs Non-Blocking

Simulator Mechanics part duo

Administrative Matters

- Readings

- Cummings SNUG Paper (*Verilog Styles that Kill*) (posted on webpage)

- Midterm: Weds Oct 25th, 7:15PM -- 9:00PM, in EH1800

- Alternate Midterm is Mon Oct 23rd, 7:15PM in ??

- Quiz Monday on Lecture04 materials

- HW2 Due in 1 week.

2

Behavioral Verilog

- Instead of describing what the hardware looks like, describe what you want the hardware to do
- Goal: Abstract away the details of the hardware implementation to make design easier
- The synthesizer creates a hardware structure that does the same thing as your description
 - ... but the synthesizer has to be able to realize your description using real hardware constraints
 - This is why not all Verilog constructs are supported

3

Behavioral Verilog

- **initial** and **always** form basis of all behavioral Verilog
 - All other behavioral statements occur within these
 - **initial** and **always** blocks cannot be nested
 - All <LHS> assignments must be to type **reg** (or **logic** if using SV)
- **initial** statements start at time 0 and execute once
 - If there are multiple **initial** blocks they all start at time 0 and execute independently. They may finish independently.
- If multiple behavioral statements are needed within the **initial** statement then the **initial** statement can be made compound with use of **begin/end**

4

More on **initial** statements

- Initial statement very useful for testbenches
- Initial statements don't synthesize
- Don't use them in DUT Verilog (stuff you intend to synthesize)

5

initial Blocks

```
'timescale 1 ns / 100 fs
module full_adder_tb;
reg [3:0] stim;
wire s, c;

full_adder iDUT(stim, carry, stim[2], stim[1], stim[0]); // instantiate DUT
// monitor statement is special - only needs to be made once,
initial $monitor("%t: s=%b c=%b stim=%b", $time, s, c, stim[2:0]);
// tell our simulation when to stop
initial #50 $stop;
initial begin // stimulus generation
    for (stim < 4'h0; stim < 4'h8; stim = stim + 1) begin
        #5;
    end
end
endmodule
```

all initial blocks start at time 0

multi-statement block enclosed by begin and end

6

Another **initial** Statement Example

```
module stim()
reg m,a,b,x,y;
initial
m = 1'b0;
initial begin
#5 a = 1'b1;
#25 b = 1'b0;
end
initial begin
#10 x = 1'b0;
#25 y = 1'b1;
end
initial
#50 $finish;
endmodule
```

What events at what times will a verilog simulator produce?

Time	Event
0	m = 1'b0
5	a = 1'b1
10	x = 1'b0
30	b = 1'b0
35	y = 1'b1
50	\$finish

7

always statements

- Behavioral block operates CONTINUOUSLY
- Executes at time zero but loops continuously
- Can use a *trigger list* to control operation; @ (a, b, c)
- In absence of a trigger list it will re-evaluate when the last <LHS> assignment completes.

```
module clock_gen (output reg clock);
initial
clock = 1'b0; // must initialize in initial block
always // no trigger list for this always
#10 clock = ~clock; // always will re-evaluate when
// last <LHS> assignment completes
endmodule
```

8

always vs initial

```
reg [7:0] v1, v2, v3, v4;
initial begin
    v1 = 1;
    #2 v2 = v1 + 1;
    v3 = v2 + 1;
    #2 v4 = v3 + 1;
    v1 = v4 + 1;
    #2 v2 = v1 + 1;
    v3 = v2 + 1;
end
```

- What values does each block produce?
 - Lets take our best guess
 - Then lets try it in ModelSim

```
reg [7:0] v1, v2, v3, v4;
always begin
    v1 = 1;
    #2 v2 = v1 + 1;
    v3 = v2 + 1;
    #2 v4 = v3 + 1;
    v1 = v4 + 1;
    #2 v2 = v1 + 1;
    v3 = v2 + 1;
end
```

9

Trigger lists (Sensitivity lists)

- Conditionally “execute” inside of **always** block
 - Any change on trigger (sensitivity) list, triggers block


```
always @(a, b, c) begin
            ...
          end
```
- Original way to specify trigger list


```
always @ (X1 or X2 or X3)
```
- In Verilog 2001 can use , instead of **or**

```
always @ (X1, X2, X3)
```
- Verilog 2001 also has * for *combinational only*

```
always @ (*)
```
- System Verilog introduced the **always_comb**

10

FlipFlops (finally getting somewhere)


- A negedge is on the transitions
 - 1 → x, z, o
 - x, z → 0
- A posedge is on the transitions
 - 0 → x, z, 1
 - x, z → 1
- Used for clocked (synchronous) logic (i.e. Flops!)

```
always @ (posedge clk)
register <= register_input;
```

Hey! What is this assignment operator?

11

Implying Flops (my way or the highway)

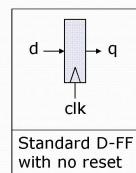

```
reg q;
always @ (posedge clk)
q <= d;
reg [11:0] DAC_val;
always @ (posedge clk)
DAC_val <= result[11:0];
```

Be careful... Yes, a non-reset flop is smaller than a reset flop, but most of the time you need to reset your flops.


Always error on the side of resetting the flop if you are at all uncertain.

12

Implying Flops (synchronous reset)

```
reg q;
always @(posedge clk)
if (!rst_n)
q <= 1'b0; //synch reset
else
q <= d;
```

How does this synthesize?

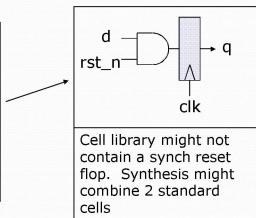


Cell library might not contain a synch reset flop. Synthesis might combine 2 standard cells

Many cell libraries don't contain synchronous reset flops. This means the synthesizer will have to combine 2 (or more) standard cell to achieve the desired function... Hmm? Is this efficient?

13

Implying Flops (asynch reset)

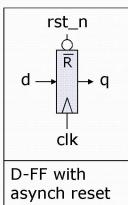

D-FF with asynch reset

```
reg q;
always @(posedge clk, negedge rst_n)
if (!rst_n)
q <= 1'b0;
else
q <= d;
```

Cell libraries will contain an asynch reset flop. It is usually only slightly larger than a flop with no reset. This is probably your best bet for most flops.

Reset has its affect asynchronous from clock. What if reset is deasserting at the same time as a + clock edge? Is this the cause of a potential meta-stability issue?

14

Know your cell library

- What type of flops are available
 - + or - edge triggered (most are positive)
 - Is the asynch reset active high or active low
 - Is a synchronous reset available?
 - Do I have scan flops available?
- Code to what is available
 - You want synthesis to be able to pick the least number of cells to implement what you code.
 - If your library has active low asynch reset flops then don't code active high reset flops.

15

What about conditionally enabled Flops?

```
reg q;
always @(posedge clk or negedge rst_n)
if (!rst_n)
q <= 1'b0; //asynch reset
else if (en)
q <= d; //conditionally enabled
else
q <= q; //keep old value
```


How does this synthesize?

How about using a gated clock?

It would be lower power right?

Be careful, there be dragons here!

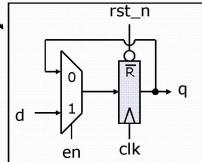Dragons you will have to face though. The benefits of clock gating (particularly power benefits) are too great to ignore just because it is "hard to do". In this class we "chicken out" and use recirculating flops style.



16

Flop Inference in System Verilog

```
module simple_ff(input clk,d,rst_n,
                  output q);
  reg q;
  always @ (posedge clk, negedge rst_n)
    if (!rst_n)
      q <= 1'b0;
    else
      q <= d;
endmodule
```

Standard verilog

System Verilog contains a type called "logic" this can be used for signals that are assigned in always blocks or in structural or dataflow.

always_ff ... no different, but Synthesis tool will warn if didn't infer a flop.

```
module simple_ff(input clk,d,rst_n,
                  output q);
  logic q;
  always_ff @ (posedge clk, negedge rst_n)
    if (!rst_n)
      q <= 1'b0;
    else
      q <= d;
endmodule
```

System verilog

In standard verilog anything assigned inside an always block must be of type `reg`.

17

Behavioral: Combinational vs Sequential

- Combinational

- Not edge-triggered
- All "inputs" (RHS nets/variables) are triggers
- Does not depend on clock

- Sequential

- Edge-triggered by clock signal
- Only clock (and possibly reset) appear in trigger list
- Can include combinational logic that feeds a FF or register

18

Blocking vs non-Blocking

- Blocking "Evaluated" sequentially
- Works a lot like software (**danger!**)
- Used for combinational logic

```
module addtree(output reg [9:0] out,
               input [7:0] in1, in2, in3, in4);
  reg [8:0] part1, part2;
  always @ (in1, in2, in3, in4) begin
    part1 = in1 + in2;
    part2 = in3 + in4;
    out = part1 + part2;
  end
endmodule
```

19

Non-Blocking Assignments

- "Updated" simultaneously if no delays given
- Used for sequential logic


```
module swap(output reg out0, out1, input rst, clk);
  always @ (posedge clk) begin
    if (rst) begin
      out0 <= 1'b0;
      out1 <= 1'b1;
    end
    else begin
      out0 <= out1;
      out1 <= out0;
    end
  end
endmodule
```

20

Swapping if done in Blocking

- Temp variable will be required
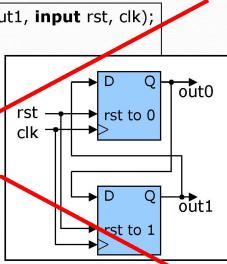
```
module swap(output reg out0, out1, input rst, clk);
reg temp;
always @(posedge clk) begin
  if (rst) begin
    out0 = 1'b0;
    out1 = 1'b1;
  end
  else begin
    temp = out0;
    out0 = out1;
    out1 = temp;
  end
end
endmodule
```




21

More on Blocking

- Called blocking because....

- The evaluation of subsequent statements <RHS> are blocked, until the <LHS> assignment of the current statement is completed.
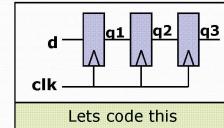
```
module pipe(clk, d, q);
input clk,d;
output q;
reg q;
always @(posedge clk) begin
  q1 = d;
  q2 = q1;
  q3 = q2;
end
endmodule
```



Lets code this


Simulate this in your head...
Remember blocking behavior of:
<LHS> assigned before
<RHS> of next evaluated.
Does this work as intended?

22

More on Non-Blocking

- Lets try that again
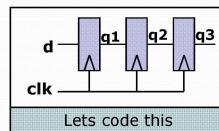
```
module pipe(clk, d, q);
input clk,d;
output q;
reg q;
always @(*)
begin
  q1 <= d;
  q2 <= q1;
  q3 <= q2;
end
endmodule;
```



Lets code this

With non-blocking statements the <RHS> of subsequent statements are **not blocked**. They are all evaluated simultaneously.

The assignment to the <LHS> is then scheduled to occur.

This will work as intended.

23

So Blocking is no good and we should always use Non-Blocking??

- Consider combinational logic

```
module ao4(z,a,b,c,d);
input a,b,c,d;
output z;
reg z,tmp1,tmp2;
always @(*)
begin
  tmp1 <= a & b;
  tmp2 <= c & d;
  z <= tmp1 | tmp2;
end
endmodule
```

The inputs (a,b,c,d) in the sensitivity list change, and the always block is evaluated.

New assignments are scheduled for tmp1 & tmp2 variables.

A new assignment is scheduled for z using the **previous** tmp1 & tmp2 values.

Does this work?

24

Why not non-Blocking for Combinational

- Can we make this example work?

```
module ao4(z,a,b,c,d);
  input a,b,c,d;
  output z;
  reg z,tmp1,tmp2;
  always @(a,b,c,d) begin
    tmp1 <= a & b;
    tmp2 <= c & d;
    z <= tmp1 | tmp2;
  end
endmodule
```

```
module ao4(z,a,b,c,d);
  input a,b,c,d;
  output z;
  reg z,tmp1,tmp2;
  always @(a,b,c,d,tmp1,tmp2) begin
    tmp1 <= a & b;
    tmp2 <= c & d;
    z <= tmp1 | tmp2;
  end
endmodule
```

What is the downside of this?

Yes
Put tmp1
& tmp2 in
the
trigger
list

25

Cummings SNUG Paper

- Posted on ECE551 website
 - Well written easy to understand paper
 - Describes this stuff better than I can
 - Read it!
- Outlines 8 guidelines for good Verilog coding
 - Learn them
 - Use them

26

Verilog Stratified Event Queue

- Need to model both parallel and sequential logic
- Need to make sure simulation matches hardware
- Verilog defines how ordering of statements is interpreted by both simulator and synthesis tools
 - Simulation matches hardware *if* code well-written
 - Can have some differences with “bad” code
 - Simulator is sequential
 - Hardware is parallel
 - Race conditions can occur

“Making it work” in
simulation does not mean
it will work after synthesis

27

Why Need to Know Event Queue

- In Behavioral Verilog, we describe the **behavior** of a circuit and the synthesizer creates hardware to try to match that behavior.
- The “**behavior**” is the input/output and timing relationships we see when simulating our HDL.
- Therefore, to understand the behavior we are describing, we must understand the order our statements will be executed in Simulation
- Because the language is designed to express parallelism, the most challenging concept is figuring out the **order that Verilog statements will occur in and how this will impact the behavior**.

28

Determinism vs Non-Determinism

- Standard guarantees some scheduling order
 - Statements in same begin-end block “executed” in the order in which they appear
 - Statements in different begin-end blocks in same simulation time have no order guarantee

```
module race(output reg f, input b, c);
  always @(*) begin
    f = b & c;
  end
  always @(*) begin
    f = b | c;
  end
endmodule
```

Race condition – which assignment to f will occur first vs. last in simulation is not known

Note that in hardware this actually models a **SHORT CIRCUIT**

29

Simulation Terminology [1]

- These only apply to SIMULATION
- Processes
 - Objects that can be evaluated
 - Includes primitives, modules, initial and always blocks, continuous assignments, tasks, and procedural assignments
- Update event
 - Change in the value of a net or register (LHS assignment)
- Evaluation event
 - Computing the RHS of a statement
- Scheduling an event
 - Putting an event on the event queue

30

Simulation Terminology [2]


- Simulation time
 - Time value used by simulator to model actual time.
- Simulation cycle
 - Complete processing of all currently active events
- Can be multiple simulation cycles per simulation time
- Explicit zero delay (#o)
 - Forces process to be inactive event instead of active
 - Incorrectly used to avoid race conditions
 - #o doesn't synthesize!
 - Don't use it

31

Verilog Stratified Event Queue [1]

- Region 1: Active Events
 - Most events except those explicitly in other regions
 - Includes \$display system tasks
- Region 2: Inactive Events
 - Processed after all active events
 - #o delay events (**bad!**)
- Region 3: Non-blocking Assign Update Events
 - Evaluation previously performed
 - Update is after all active and inactive events complete
- Region 4: Monitor Events
 - Caused by \$monitor and \$strobe system tasks
- Region 5: Future Events
 - Occurs at some future simulation time
 - Includes future events of other regions
 - Other regions only contain events for CURRENT simulation time

32

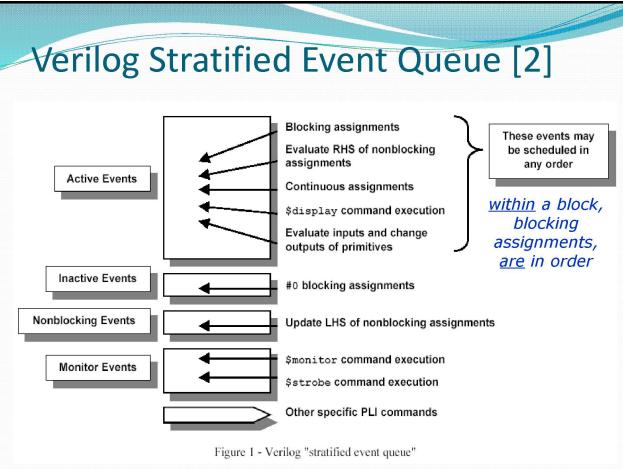

Simulation Model

```

Let T be current simulation time
while (there are events) {
    if (no active events) {
        if (inactive events) activate inactive events
        else if (n.b. update events) activate n.b. update events
        else if (monitor events) activate monitor events
        else { advance T to the next event time
            activate all future events for time T }
    }
    E = pull event from event queue
    if (E is an update event) {
        update the modified object
        add evaluation events for sensitive processes to the event queue
    } else {
        evaluate the process // evaluation event (of non-blocking)
        add update event(s) to the event queue
    }
}

```

34

Race Condition

```

assign p = q;
initial begin
    q = 1;
    #1 q = 0;
    $display(p);
end

```

- What is displayed?
- What if **\$strobe(p)** were used instead?

35

Hand Simulation of:

Active:	NB Update:	Future:
p = x		#1 q = 0, \$display(p)
q = 1		
p = 1		
q = 0, \$display(p)		
p = 0		

```

assign p = q;
initial begin
    q = 1;
    #1 q = 0;
    $display(p);
end

```

Time	Event/Action
0	p = x
0	q = 1
0	p = 1
1	q = 0
1	\$display(1)
1	p = 0

36

Simulate This by Hand

```

always @(posedge clk, negedge rst_n)
  if (!rst_n)
    FF1 <= 1'b0
  else
    FF1 <= d;

always @(posedge clk)
  FF2 <= FF1;

initial begin
  clk = 0;
  rst_n = 0;
  d = 1;
  #5 rst_n = 1;
  #5 clk = 1;
end

```

- Show queues vs time for:
- Active events
 - Update events
 - Future events

37

Hand Simulation of:

Active:	NB Update:	Future:
clk = 0	FF1 <= 0	#5 rst_n = 1
rst_n = 0	FF1 <= 1	#5 clk = 1
d = 1	FF2 <= 0	
always_FF1		
FF1 = 0		
rst_n = 1		
clk = 1		
always_FF1		
always_FF2		
FF1 = 1		
FF2 = 0		

```

always @(posedge clk, negedge rst_n)
  if (!rst_n)
    FF1 <= 1'b0
  else
    FF1 <= d;

always @(posedge clk)
  FF2 <= FF1;

initial begin
  clk = 0;
  rst_n = 0;
  d = 1;
  #5 rst_n = 1;
  #5 clk = 1;
end

```

Time	Event/Action
0	clk = 0
0	rst_n = 0
0	d = 1
5	rst_n = 1
10	Clk = 1
10	FF1 = 1
10	FF2 = 0

38

What Do I Need to Know?

- Don't need to memorize
 - Exact Simulation model
 - The process of activating events from a region
- Do need to understand
 - Order statements are evaluated
 - Active, Non-Blocking, and Monitor regions
 - \$display vs. \$strobe vs. \$monitor
 - Separation of evaluation and update of non-blocking
- Midterm will have a question related to event queue

39

if...else if...else statement

- General forms...

```

if (condition) begin
  <statement1>;
  <statement2>;
end

```

Of course the compound statements formed with **begin/end** are optional.

Multiple else if's can be strung along indefinitely

```

if (condition)
begin
  <statement1>;
  <statement2>;
end
else
begin
  <statement3>;
  <statement4>;
end

```

```


if (condition)
begin
  <statement1>;
  <statement2>;
end
else if (condition2)
begin
  <statement3>;
  <statement4>;
end
else
begin
  <statement5>;
  <statement6>;
end

```

40

How does and if...else if...else statement synthesize?

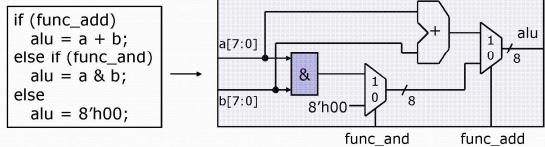- Does not conditionally “execute” block of “code”
- Does not conditionally create hardware!
- It makes a multiplexer or selecting logic
- Generally:
 - ✓ Hardware for both paths is created
 - ✓ Both paths “compute” simultaneously
 - ✓ The result is selected depending on the condition




41

if statement synthesis (continued)

```
if (a)
  func = c & d;
else if (b)
  func = c | d;
```

How does this synthesize?

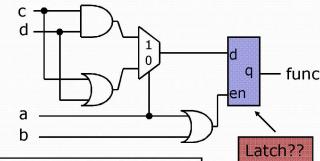

What you ask for is what you get!

func is of type register. When neither **a** or **b** are asserted it didn't get a new value.

That means it must have remained the value it was before.

That implies memory...i.e. a **latch**!

Always have an **else** to any **if** to avoid unintended latches.

42

Latch Avoidance in System Verilog

```
reg func;
always @ (a,b,c,d)
  if (a)
    func = c & d;
  else if (b)
    func = c | d;
```

Traditional verilog

Produces a latch, but gives no warning (unless `hdlin_check_no_latch` is set true).

`func` has to be of type `reg` even though intent is not to infer a sequential element.

```
logic func;
always_comb
  if (a)
    func = c & d;
  else if (b)
    func = c | d;
```

System verilog

Produces a latch, but gives warning since always block said we intended combinational. No sensitivity list needed.

`func` can be of type `logic`, which makes more sense than `reg`.

43

More on if statements...

- Watch the sensitivity lists...what is missing in this example?

```
always @ (a, b) begin
  temp = a - b;
  if ((temp < 8'b0) && abs)
    out = -temp;
  else out = temp;
end
```

```
always @ (posedge clk) begin
  if (reset) q <= 0;
  else if (set) q <= 1;
  else q <= data;
end
```

What is being coded here?

Is it synchronous or asynch?

Does the reset or the set have higher priority?

44

Example: Comparator

```
module compare_4bit_behavior(output reg A_lt_B, A_gt_B, A_eq_B,
                             input [3:0] A, B);
    always@( A,B ) begin
        /////////////////////////////////////////////////////////////////// default outputs to prevent latches ///////////////////////////////////////////////////////////////////
        A_lt_B = 0;
        A_gt_B = 0;
        A_eq_B = 0;
        if (A==B)
            A_eq_B = 1;
        else if (A<B)
            A_lt_B = 1;
        else
            A_gt_B = 1;
    end
endmodule
```

Flush out this template with sensitivity list and implementation
Hint: a...else if...else statement works well for implementation

45

Example: Comparator

```
module compare_4bit_behavior(output reg A_lt_B, A_gt_B, A_eq_B,
                             input [3:0] A, B);
    always@( A,B ) begin
        if (A==B) begin
            A_lt_B = 0;
            A_eq_B = 1;
            A_gt_B = 0;
        end else if (A<B) begin
            A_lt_B = 1;
            A_eq_B = 0;
            A_gt_B = 0;
        end else begin
            A_lt_B = 0;
            A_eq_B = 0;
            A_gt_B = 1;
        end
    end
endmodule
```

46

case Statements

- Verilog has three types of case statements:
 - case**, **casex**, and **casez**
- Performs bitwise match of expression and case item
 - Both must have same bitwidth to match!
- case**
 - Can detect x and z! (good for testbenches)
- casez**
 - Uses z and ? as “don’t care” bits in case items and expression
- casex**
 - Uses x, z, and ? as “don’t care” bits in case items and expression

47

Case statement (general form)

```
case (expression)
  alternative1 : statement1;           // any of these statements could
  alternative2 : statement2;           // be a compound statement using
  alternative3 : statement3;           // begin/end
  default : statement4;               // always use default for synth stuff
endcase
```

```
localparam AND = 2'b00;
localparam OR = 2'b01;
localparam XOR = 2'b10;

case (alu_op)
  AND      : alu = src1 & src2;
  OR       : alu = src1 | src2;
  XOR      : alu = src1 ^ src2;
  default   : alu = src1 + src2;
endcase
```

Why always have a default?

Same reason as always having an else with an if statement.

All cases are specified, therefore no unintended latches.

48

Using case To Detect x And z

- Only use this functionality in a testbench!
- Example taken from Verilog-2001 standard:

```
case (sig)
  1'bz:      $display("Signal is floating.");
  1'bx:      $display("Signal is unknown.");
  default:   $display("Signal is %b.", sig);
endcase
```

49

casex Statement

- Uses x, z, and ? as single-bit wildcards in case item and expression
- Uses first match encountered

```
always @ (code) begin
  casex (code)
    2'b0?: control = 8'b00100110; // case item1
    2'b10: control = 8'b11000010; // case item 2
    2'b11: control = 8'b00111101; // case item 3
  endcase
end
```

- What is the output for code = 2'b01
- What is the output for code = 2'b1x

50

casez Statement

- Uses z, and ? as single-bit wildcards in case item and expression

```
always @ (code) begin
  casez (code)
    2'b0?: control = 8'b00100110; // item 1
    2'bz1: control = 8'b11000010; // item 2
    default: control = 8b'xxxxxxxx; // item 3
  endcase
end
```

- What is the output for code = 2b'01
- What is the output for code = 2b'zz

51


How Does a case(x) Statement Synthesize?

Remember the First Match is taken
(*there is an inferred priority*)

```
always @((sel,a,b,c)
  case (sel)
    2'b00 : out = a;
    2'b01 : out = b;
    default : out = c;
  endcase;
```

Synthesis Tool

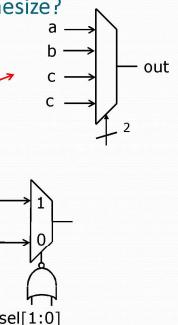
Depends on several factor including some synthesis directives. However the 2nd case is what we expect it to do without any directives. System verilog gives us more control.




52

System Verilog Case Options
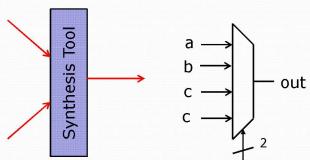
```
always @(sel,a,b,c)
unique case (sel)
 2'b00 : out = a;
 2'b01 : out = b;
 default : out = c;
endcase;
```


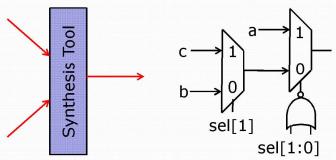
```
always @(sel,a,b,c)
priority case (sel)
 2'b00 : out = a;
 2'b01 : out = b;
 default : out = c;
endcase;
```



53