

ECE 551

Exercise02

This is a 10pt problem of HW1

Submit whatever you have for both the DUT and test results to the dropbox by end of the class period.

Submit a **structural** Verilog file that models a module that can synchronize a signal to a your system clock (**clk**) and output a signal that is high for 1 clock cycle when that signal has a falling edge. Assume a D-FF is already defined that has an interface of:(D, clk,Q) and a module name of **dff**.

So essentially a circuit to solve metastability, then detect a falling edge.

Name your file **synch_detect.v** and ensure the module name is also **synch_detect**.

Interface is:

asynch_sig_in → input to synchronize and detect falling edge on

clk → clock signal

fall_edge → output of your block that is high for 1 clock cycle after falling edge occurs on asynch_sig_in.

The code for **dff.v**, and a testbench are provided (**synch_detect_tb.v**) are provided in the Exercise02 folder on Moodle.

Create a ModelSim project, download, and test your design. The test bench is self checking and should give a happy message in the console window if your DUT is good.